

Université d'Ottawa  
Faculté de génie

École de science informatique  
et de génie électrique



University of Ottawa  
Faculty of Engineering

School of Electrical Engineering  
and Computer Science

## **ELG4137 Winter 2023 Assignment 1**

**Constantine Valettas #300027819**

The following document indicates the size of the transistors (W/L) and the reasoning behind why they were used in the NAND logic gate design.

Gate size - defined as...

$$\text{Gate size} = \frac{R}{\underbrace{\text{largest fall or largest rise resistance}}_{\text{designed to be equal}}}$$


if Gate size = 1

Then the sizes of the Nmos & Pmos transistors are selected to ensure that the largest rise & fall resistance is equal to R

→ according to the formula for Gate size, we need to increase transistor size from 1 to 2.


Doing so will change the pull down resistance to  $R/2$  &  $R/2$ .

 $R/2 + R/2 = R \rightarrow \therefore$  the formula for gate size is satisfied



Calculating W/L ratio of a transistor

CMOS NAND Gate

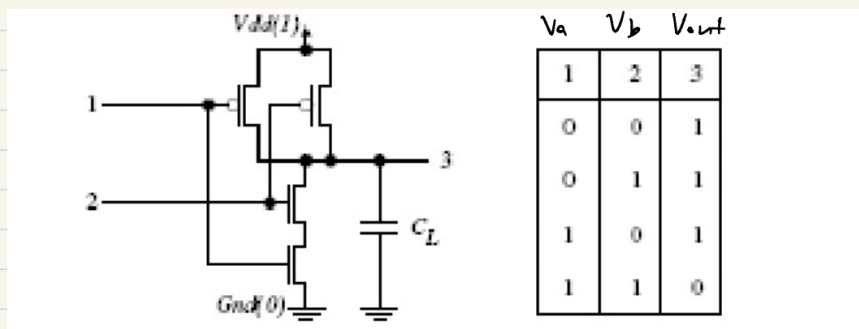

→ we have 2 pmos transistors in parallel & 2 nmos transistors in series

$$\left(\frac{W}{L}\right)_{\text{eff}} \text{ of nmos} = \frac{1}{1}$$

→ 2 nmos transistors in series (consider 2 ratios)

$$\frac{1}{1} = \frac{1}{\frac{L}{W} + \frac{L}{W}}$$

$$\frac{1}{1} = \frac{1}{\frac{2L}{W}}$$

$$\frac{1}{1} = \frac{W}{2L}$$

$$\frac{1}{1} = \frac{W}{L} \cdot \frac{1}{2}$$

$$\frac{1}{\frac{1}{2}} = \frac{W}{L} \rightarrow \frac{1}{1} \times 2 = \frac{W}{L}$$

$$\rightarrow \boxed{\frac{2}{1} = \frac{W}{L}}$$

∴ the ratio of the  $\frac{W}{L}$  for the nmos transistor is  $\frac{2}{1}$

For PMOS

From before, we know that,

$$\frac{2}{1} = \left(\frac{W}{L}\right)_{\text{eff}}$$

→ pmos transistors in parallel

$$\frac{2}{1} = \frac{1}{\frac{L}{W}} \rightarrow \frac{2}{1} = \frac{W}{L}$$

∴ the ratio  $\frac{W}{L}$  for the pmos transistor is  $\frac{2}{1}$

Since we now know the transistor  $\frac{W}{L}$  ratios, we can implement certain sizes into verituous L design.

→ Since smaller transistor sizes offer several benefits such as improved performance (faster switching speeds & lower power consumption), I have chosen transistor width of 200 nm & length of 100 nm

To observe the different ways in which the output of the gate rises to 1 or falls to 0, let's take a look at a NAND2 logical gate truth table


2 - input NAND gate



A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

When both inputs are 0, the output is 1. When either input has a value of 1, the output is also 1. Lastly, when both inputs are 1, the output is 0.

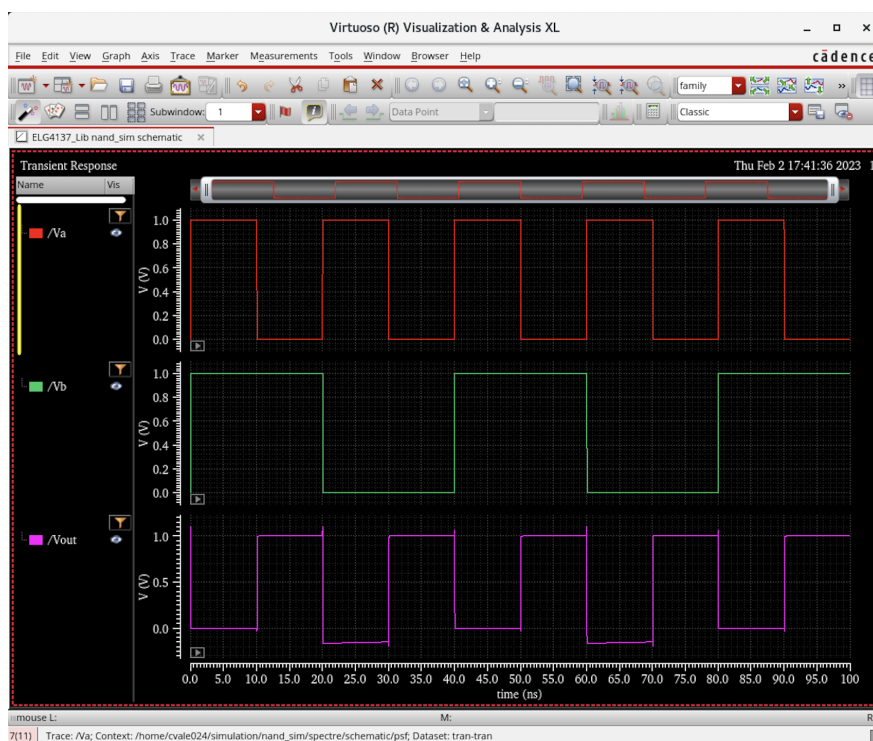Now let's take a look at our testbench simulation for input values 0 or Vdd, for comparison.



From this simulation we can see that when  $V_a = 0$ ,  $V_b = 0$ , and  $V_{out} = 1$

When  $V_a = 0$ ,  $V_b = 1$ , and  $V_{out} = 1$

When  $V_a = 1$ ,  $V_b = 0$ , and  $V_{out} = 0$ . This is incorrect as  $V_{out}$  should be 1.

When  $V_a = 1$ ,  $V_b = 1$ , and  $V_{out} = 0$ .

After comparing the simulation to the NAND truth table, all of the cases are correct except for one. Therefore, the gate is non-conclusive and the gate cannot be verified as a properly operating NAND gate.

The virtuoso schematic files have been added to the zipped folder this pdf document is in. Below are just some screenshots.

